

Write the voltage drop for the following circuit elements:

1. resistor
2. capacitor
3. inductor