

Write down the power dissipated by a resistor.