

Write the impedance for a

1. capacitor
2. inductor
3. resistor

State the formula for the equivalent impedance for impedances in

1. series
2. parallel