

Write down Kirchhoff's rules for currents and voltage drops.